

Glow Plug Circuit Diagnostic Checklist

Diagnosis: Solving Hard Cold Starts

SYMPTOM

Engine cranks but won't fire, or starts very roughly with lots of white smoke, only when cold.

STEP 1 – Observe the Dashboard Glow Plug Light

- Light never comes on → Control circuit fault (fuse, relay, wiring, dashboard bulb).
- Light stays on for a very short time when very cold → Faulty temperature sensor or control unit.
- Light behaves normally → Control system likely OK. Proceed to glow plugs and power circuit.

STEP 2 – Glow Plug Resistance Test (Best Test)

- Disconnect the main bus bar or wire linking all glow plugs.
- Set multimeter to Ohms (Ω).
- Measure between glow plug terminal and engine ground.

Healthy Reading: 0.5Ω – 2.0Ω (all cylinders should read similarly).

Bad Readings:

- Infinite / OL → Open circuit (dead glow plug).
- $> 5\Omega$ → Weak glow plug (slow or ineffective heating).
- 0.00Ω → Short circuit (rare but possible).

STEP 3 – Power Circuit Test

- Listen for relay "CLUNK" when key is turned to ON.
- While glow plug light is ON, check for 12V at the glow plug bus bar.
- No voltage → Relay, fuse, or feed wire fault.

STEP 4 – Quick Test (Use With Caution)

- Disconnect fuel cut-off solenoid before cranking.
- Use heavy jumper wire from battery (+) to glow plug terminal.
- Good glow plug heats within 5–10 seconds.
- No heat → Glow plug or connection is faulty.

Pro Tips & Common Failures

- Glow plugs fail as a set – replacing all is recommended.
- Glow plug relay failure is very common.
- Battery health is critical for cold starts.

- White smoke = unburned fuel (possible low compression or injector issue).

Want the FULL Diesel Cold-Start Diagnostic eBook (PDF)?

Visit: helpymechanic.com